


Computer-Aided VLSI System Design

Homework 2: Simple MIPS CPU

Graduate Institute of Electronics Engineering, National Taiwan University




NTU GIEE

 

Goal

 - In this homework, you will learn
 - How to write testbench
 - How to design FSM
 - How to use IP
 - Generate patterns for testing





Introduction

- Central Processing Unit (CPU) is one of the most important core in a computer system. In this homework, you are asked to design a simple CPU which consists of a program counter, an ALU, and a register file. The instruction set of the simple CPU is similar to MIPS ISA (Instruction Set Architecture).


Instruction set

 
```
addi $7 $3 4
sub  $7 $7 $5
sw   $7 $4 8
bne  $3 $5 12
lw   $6 $0 8
add  $7 $6 $2
sw   $7 $4 8
eof
```



 


Block Diagram

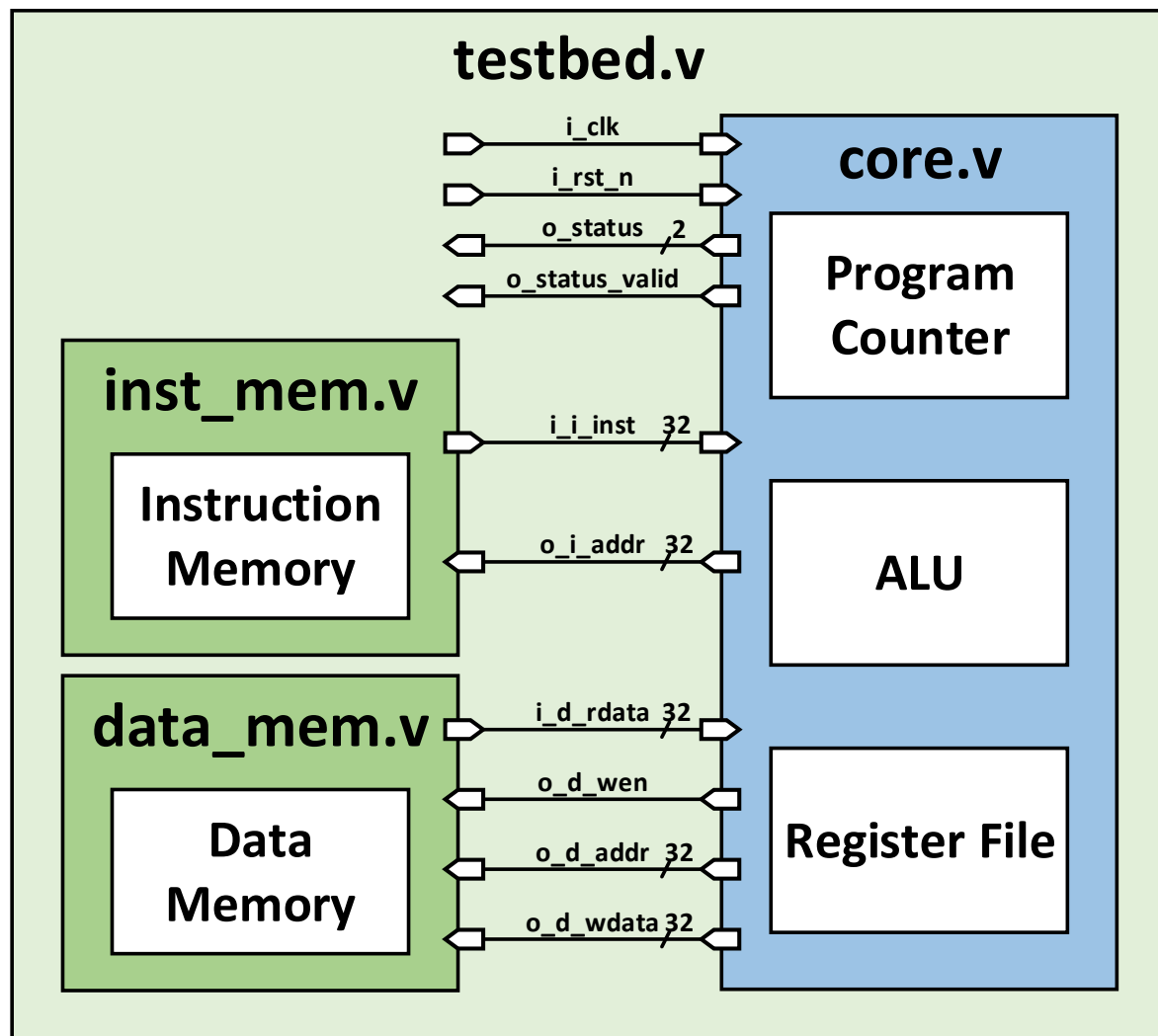

 


Input/Output

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system.
i_rst_n	I	1	Active low asynchronous reset.
o_i_addr	O	32	Address from program counter (PC)
i_i_inst	I	32	Instruction from instruction memory
o_d_wen	O	1	Write enable of data memory Set low for reading mode, and high for writing mode
o_d_addr	O	32	Address for data memory
o_d_wdata	O	32	Data input to data memory
i_d_rdata	I	32	Data output from data memory
o_status	O	2	Status of the core after processing each instruction
o_status_valid	O	1	Set high if ready to output status

 


Specification (1)

- All outputs should be synchronized at clock **rising** edge.
- You should set all your outputs and register file to be zero when `i_rst_n` is **low**. Active low asynchronous reset is used.
- Instruction memory and data memory are provided. All values in memory are reset to be zero.
- You should create **32 registers (each register is 32-bit)** in register file.
- After outputting `o_i_addr` to instruction memory, the core can receive the corresponding `i_i_inst` at the next rising edge of the clock.

 


Specification (2)

- To load data from the data memory, set o_d_wen to **0** and o_d_addr to relative address value. i_d_rdata can be received at the next rising edge of the clock.
- To save data to the data memory, set o_d_wen to **1**, o_d_addr to relative address value, and o_d_wdata to the written data. At the next rising of the clock, the data is written to memory.
- Your o_status_valid should be set to **high** for only **one cycle** for every o_status.
- The testbench will get your output at negative clock edge to check the o_status if your o_status_valid is **high**.

 

Specification (3)


- When you set o_status_valid to **high** and o_status to **3**, stop processing. The testbed will check the data in data memory with golden data.
- If overflow happens, stop processing and raise o_status_valid to **high** and set o_status to **2**. The testbed will check the data in data memory with golden data.
- Less than **1024** instructions are provided for each pattern.
- The whole processing time can't exceed **120000** cycles.

 


Program Counter

- Program counter is used to control the address of instruction memory.

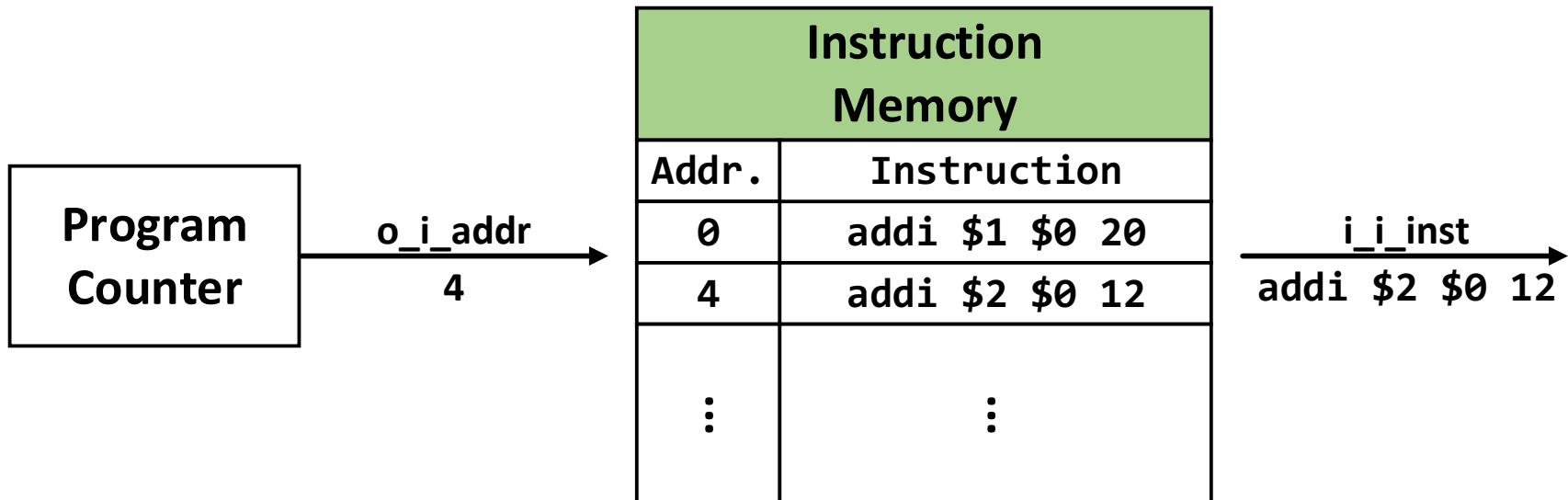
$\$pc = \$pc + 4$ for every instruction (except for **beq**, **bne**)



 


Instruction mapping


■ R-type

 


■ I-type

 

■ EOF

 


 

Instruction

Operation	Assemble	Opcode	Type	Meaning	Note
Add	add	6'd1	R	$\$s1 = \$s2 + \$s3$	Signed operation
Subtract	sub	6'd2	R	$\$s1 = \$s2 - \$s3$	Signed operation
Add unsigned	addu	6'd3	R	$\$s1 = \$s2 + \$s3$	Unsigned operation
Subtract unsigned	subu	6'd4	R	$\$s1 = \$s2 - \$s3$	Unsigned operation
Add immediate	addi	6'd5	I	$\$s1 = \$s2 + im$	Signed operation
Load word	lw	6'd6	I	$\$s1 = Mem[\$s2 + im]$	Unsigned operation
Store word	sw	6'd7	I	$Mem[\$s2 + im] = \$s1$	Unsigned operation
AND	and	6'd8	R	$\$s1 = \$s2 \& \$s3$	Bit-wise
OR	or	6'd9	R	$\$s1 = \$s2 \$s3$	Bit-wise
NOR	nor	6'd10	R	$\$s1 = \sim(\$s2 \$s3)$	Bit-wise
Branch on equal	beq	6'd11	I	if($\$s1 == \$s2$), $\$pc = \$pc + 4 + im$; else, $\$pc = \$pc + 4$	PC-relative Unsigned operation
Branch on not equal	bne	6'd12	I	if($\$s1 \neq \$s2$), $\$pc = \$pc + 4 + im$; else, $\$pc = \$pc + 4$	PC-relative Unsigned operation
Set on less than	slt	6'd13	R	if($\$s2 < \$s3$), $\$s1 = 1$; else, $\$s1 = 0$	Signed operation
End of File	eof	6'd14	EOF	Stop processing	Last instruction in the pattern

Note: Use two's complement arithmetic for signed operations.

 


Memory IP

- Instruction memory
 - Size: 1024×32 bit
 - `i_add[11:2]` for address mapping in instruction memory
- Data memory
 - Size: 64×32 bit
 - `i_add[7:2]` for address mapping in data memory

```
module inst_mem (  
    input          i_clk,      // 1-bit  
    input          i_rst_n,    // 1-bit  
    input [ 31 : 0 ] i_addr,    // 32-bit  
    output [ 31 : 0 ] o_inst    // 32-bit  
);
```

 
```
module data_mem (  
    input          i_clk,      // 1-bit  
    input          i_rst_n,    // 1-bit  
    input          i_wen,      // 1-bit  
    input [ 31 : 0 ] i_addr,    // 32-bit  
    input [ 31 : 0 ] i_wdata,   // 32-bit  
    output [ 31 : 0 ] o_rdata   // 32-bit  
);
```



Status


- 4 types of o_status

o_status[1:0]	Definition
2'd0	R_TYPE_SUCCESS
2'd1	I_TYPE_SUCCESS
2'd2	MIPS_OVERFLOW
2'd3	MIPS_END

 


Overflow

- Overflow may happen
 - **Situation1**: Overflow happens at arithmetic instructions (add, sub, addu, subu, addi)
 - **Situation2**: The address of data/instruction memory is out of the memory size (Do not consider the case if instruction address is beyond eof, but the address mapping is still in the size of instruction memory)
- Once an overflow happens, the testbed stops and checks the data memory

 


Waveform

■ Status Check

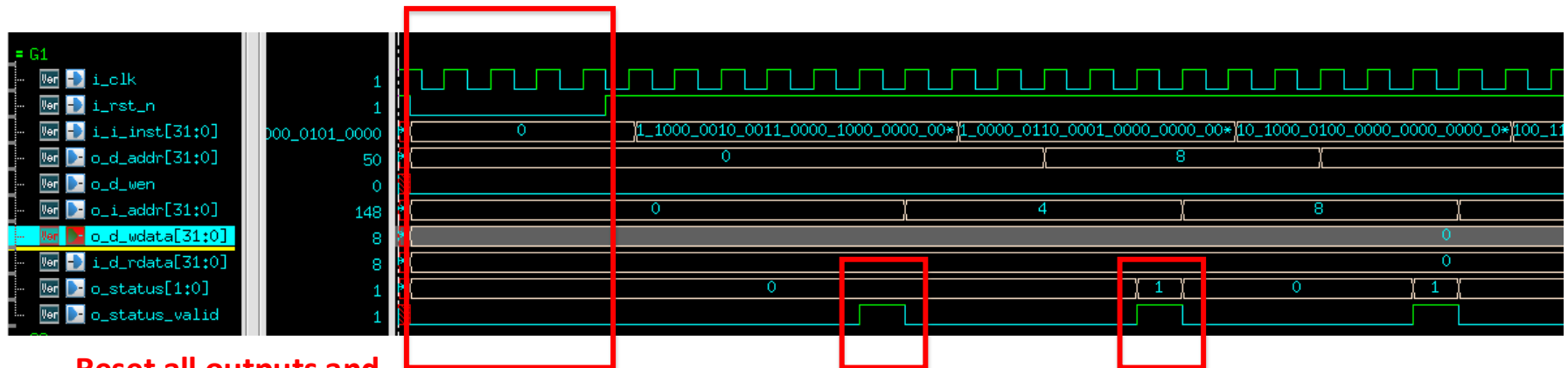


Reset all outputs and
register file to 0

 
o_status is 0 if R-type instruction success,
 o_status is 1 if I-type instruction success



Waveform


■ Status Check

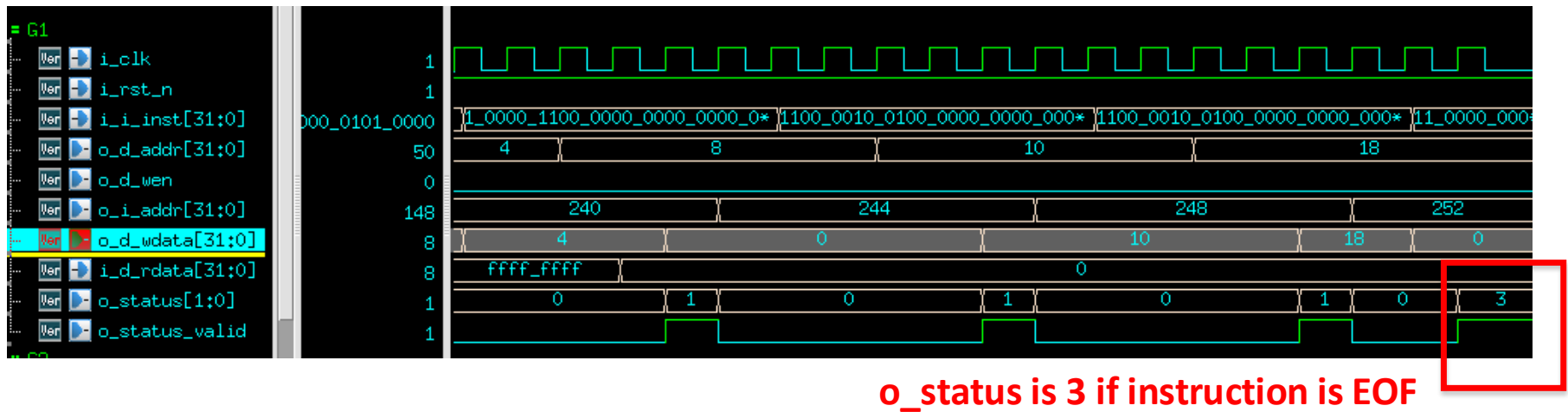

 


Waveform

 - Read instruction from instruction memory




Output `o_i_addr` for relative instruction →

 ← Get `i_i_inst` at the next rising edge of clock




Waveform

- Load data from data memory

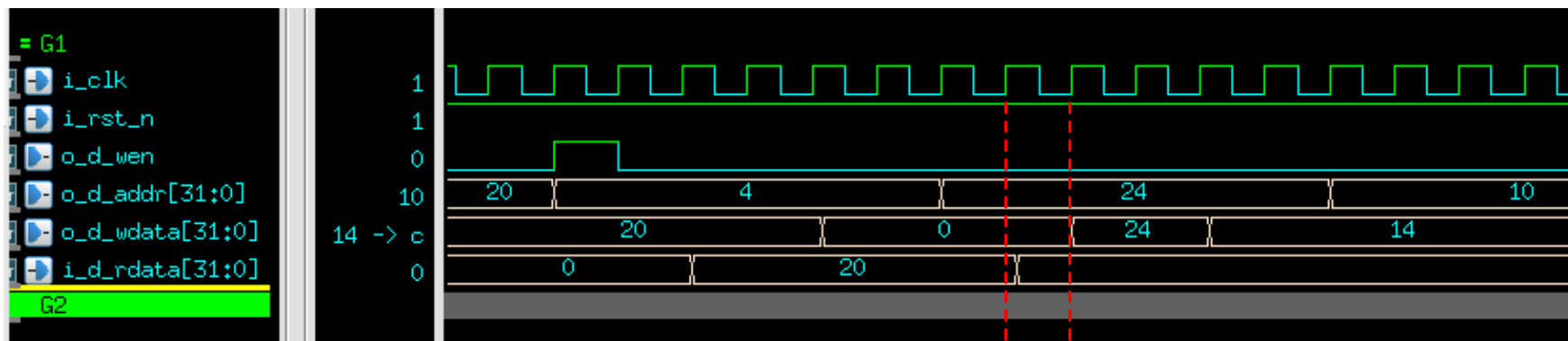


`o_d_wen` = 0, load data from data memory at `o_d_addr` = 24

 Receive `i_d_rdata` at next rising edge of clock




Waveform

- Save data to data memory

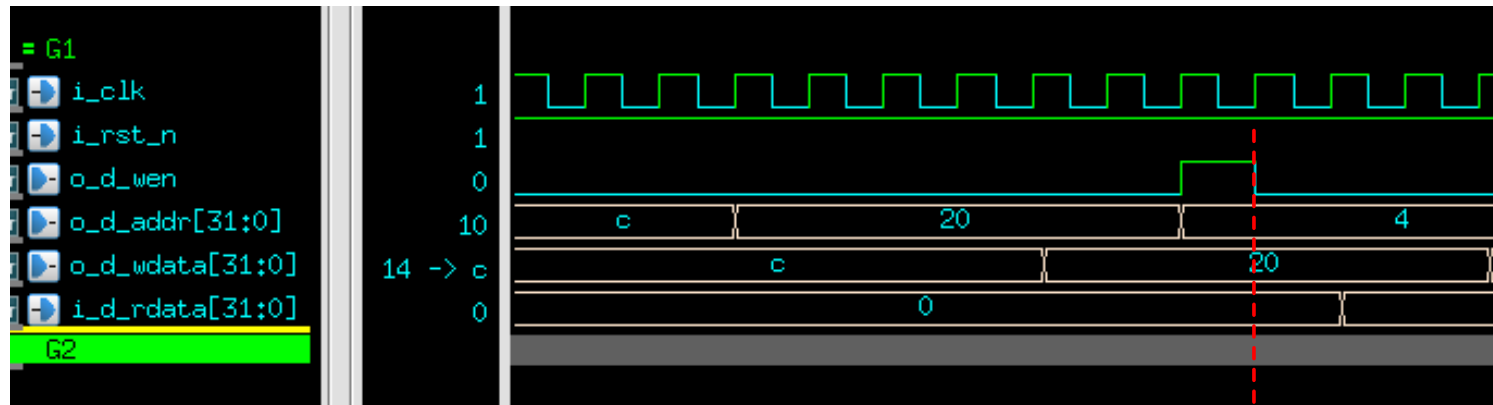


 **`o_d_wen = 1`, store `o_d_wdata`
to data memory at `o_d_addr = 4`**



core.v


```
module core #(                                //Don't modify interface
    parameter ADDR_W = 32,
    parameter INST_W = 32,
    parameter DATA_W = 32
)(
    input                i_clk,
    input                i_rst_n,
    output [ ADDR_W-1 : 0 ] o_i_addr,
    input  [ INST_W-1 : 0 ] i_i_inst,
    output                o_d_wen,
    output [ ADDR_W-1 : 0 ] o_d_addr,
    output [ DATA_W-1 : 0 ] o_d_wdata,
    input  [ DATA_W-1 : 0 ] i_d_rdata,
    output [          1 : 0 ] o_status,
    output                o_status_valid
);
```

 

rtl.f

- Filelist
 
```
// -----  
// Simulation: HW2 simple mips CPU  
// -----  
  
// define files  
// -----  
../00_TESTBED/define.v  
  
// testbench  
// -----  
../00_TESTBED/testbed.v  
../00_TESTBED/inst_mem.vp  
../00_TESTBED/data_mem.vp  
  
// design files  
// -----  
./core.v
```




Command

- 01_run

```
ncverilog -f rtl.f +define+p0 +access+rw
```


- 99_clean_up
 
```
rm -rf INCA_libs/ ncverilog.* novas*
```



define.v

```
1  // opcode definition
2  `define OP_ADD  1
3  `define OP_SUB  2
4  `define OP_ADDI 3
5  `define OP_LW   4
6  `define OP_SW   5
7  `define OP_AND  6
8  `define OP_OR   7
9  `define OP_NOR  8
10 `define OP_BEQ  9
11 `define OP_BNE 10
12 `define OP_SLT  11
13 `define OP_EOF  12
14
15 // MIPS status definition
16 `define R_TYPE_SUCCESS 0
17 `define I_TYPE_SUCCESS 1
18 `define MIPS_OVERFLOW 2
19 `define MIPS_END 3
20
```

 

testbed_temp.v

- Things to add in your testbench
 - Clock
 - Reset
 - Waveform file
 - Function test
 - ...

```
module testbed;


    wire clk, rst_n;
    wire [ 31 : 0 ] imem_addr;
    wire [ 31 : 0 ] imem_inst;
    wire          dmem_wen;
    wire [ 31 : 0 ] dmem_addr;
    wire [ 31 : 0 ] dmem_wdata;
    wire [ 31 : 0 ] dmem_rdata;
    wire [ 1 : 0 ] mips_status;
    wire          mips_status_valid;

    initial $readmemb (`Inst, u_inst_mem.mem_r); // Don't modify
```

```
core u_core (
    .i_clk(),
    .i_rst_n(),
    .o_i_addr(),
    .i_i_inst(),
    .o_d_wen(),
    .o_d_addr(),
    .o_d_wdata(),
    .i_d_rdata(),
    .o_status(),
    .o_status_valid()
);

inst_mem u_inst_mem (
    .i_clk(),
    .i_rst_n(),
    .i_addr(),
    .o_inst()
);

 data_mem u_data_mem (
    .i_clk(),
    .i_rst_n(),
    .i_wen(),
    .i_addr(),
    .i_wdata(),
    .o_rdata()
);
```





Protected Files

- The following files are protected
 - inst_mem.vp
 - data_mem.vp

```
module inst_mem (
    input          i_clk,
    input          i_rst_n,
    input  [ 31 : 0 ] i_addr,
    output [ 31 : 0 ] o_inst
);
`protected
Nd15kSQH5DT^<D9i:i7T7ceFn3@o:C2]Ke:L;dfq^QGQOG?3K:ogIe8]1ge<gcg3
lCH3E]ekmLN<RVkKa1o39E7E21a;`hJRSFMUb2pAgL?TeZdH>]^RK;KWYU@>G2G6
H[IMYG;D<[Z>;0`?NbPoEAQM<_ZfDbp1HN@HmqS0`Q<5[53C:9UD4^:Y44]9a^e
PDH[cdHb;HPi\R4k7mA1PdY8ZpI=4?nNZgQ2I>QUg[agM4j@cT1]hnMoC<i1F9DR
[kf;]ULlecpF`H;9L2DeZa>@LdfLgfb814bwgT:_P3?ENhifQW@_Ne;gMZE9@f0A
OERY:F4d68KqAIn]N1dj4LN7_8:Uigk?9UJ9JYQM4l=Lq\TEXDQ01>Zo^Sjq=Cge
?kp68am:9p81Q1[<jSXm?;GhoPHHYKp\Q][2epXn_18k8LA5g=N7=D?=VOX<Ham8
[A:Qc;Rlp038>d9_Qk9cfk?:5hXP>LT3n=DP08A_]WPa6nA3cYZjG132qB9]I4kp
>=:4m9P`dCB8@?ip`@VR7AahIggjNR:M1:_\KXE1BF0m<Bb@ZS[^W7EheJ18mX8;
?7F`Pg\CCA8igfFUoWY@k>Yq=U3_4>E50_nJ\`aUGcfWD_89dab]cUQFF<?2P?OG
qWglWC[\iqnjC<OipHHnb<T4Sg<:UORVSVocI_g?<a@o__<PQ493cZIE;7^Sp1AQ
G<c17[ ]R\>VT]]LA\7?Uk=]\bG19MT9N;K<Y92[iK0ged92EIkQZliw>q1G]QI?5
ST06RFN<KJl@VM1EWKSmb1B5U:BaX`E7of7mq0JBg0`9k$
`endprotected

endmodule
```

 


PATTERN

- Files in PATTERN are for your references

inst_assemble.dat
 
```
-----  
R-type  $s2  $s3  $s1  
I-type  $s2  $s1  im  
-----  
and      $1    $3    $1  
lw       $3    $1     8  
bne      $2    $0     8  
add      $7    $1    $4  
slt      $6    $5    $4  
slt      $4    $1    $1  
lw       $1    $3    12  
lw       $7    $7     4  
bne      $6    $7     8  
lw       $6    $5     8  
lw       $5    $2     8
```




Error Messages

- Wrong status

```
-----  
Pattern: ../00_TESTBED/PATTERN/p0/inst.dat  
-----  
MIPS Status Error! Status[          2]: Golden = 01, Yours = 11
```

- Wrong data

 
```
-----  
Pattern: ../00_TESTBED/PATTERN/p0/inst.dat  
-----  
Error! Data[          0]: Golden = 00000002, Yours = 00000000  
Total error:          1
```



Grading Policy

- TA will run your code with the following command


```
ncverilog -f rtl.f +define+p0 +access+rw
```
- Pass the patterns to get full score
 - Provided pattern: **80%**
 - **40%** for each test (data from data memory: **20%**, status check: **20%**)
 - Hidden pattern: **20%** (20 patterns in total)
 - **1%** for each test (data & status both correct)
- Delay submission
 - - In one day: **(original score)*0.6**
 - - In two days: **(original score)*0.3**
 - - More than two days: **0 point** for this homework
- Lose **3 points** for any wrong naming rule or format for submission

 

Submission

- Create a folder named **studentID_hw2**, and put all below files into the folder
 - **rtl.f** (your file list)
 - **core.v**
 - **all other design files** in your file list (optional)

 - Compress the folder **studentID_hw2** in a tar file named **studentID_hw2_vk.tar** (k is the number of version, $k = 1, 2, \dots$)



Hint

- Design your FSM with following states
 1. Idle
 2. Instruction Fetching
 3. Instruction decoding
 4. ALU computing/ Load data
 5. Data write-back
 6. Next PC generation
 7. Process end